

Question [1]: [25 mark]

- a) Using a suitable decoder and 3 logic gates, design a logic circuit that adds two 2-bit numbers, $N_1=A_1A_0$ and $N_2=B_1B_0$, Where N_1 is the MS and N_2 is the LS. Carry in is zero (no carry in) (for example $N_1=10$, $N_2=11$, $N_1+N_2=101=C_{out}S_2S_1$, $C_{out}=\text{Carry out}=1$, $S_2=\text{Sum2}=0$, $S_1=\text{Sum1}=1$) (Hint: Construct the truth table to find the logic expressions of C_{out} , S_2 and S_1 in decimal minterms notation, then design the required circuit)
- b) Design a circuit for C_{out} using multiplexer and some logic gates as required. Use A_1 and A_0 as select inputs.

Q1) Test 2


a)

A_1	A_0	B_1	B_0	C_0	S_2	S_1
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0


$S_1 = \sum m(1, 3, 4, 6, 9, 11, 12, 14)$
 $S_2 = \sum m(2, 3, 5, 6, 8, 9, 12, 15)$
 $C_0 = \sum m(7, 10, 11, 13, 14, 15)$

③

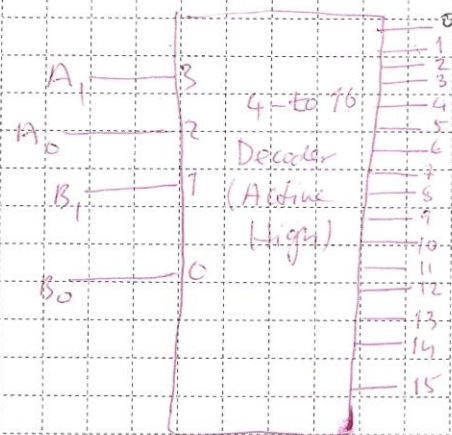AS.A Dr. Waad
This is the solution of Q1 -
M.A



10

 


b)

$$C_0 = \sum m(7, 10, 11, 13, 14, 15)$$

$A_1 A_0$	I_0	I_1	I_2	I_3
$B_1 B_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	1	1	1
10	0	0	1	1

$I_0 = 0$
 $I_1 = B_0 B_1$
 $I_2 = B_1$
 $I_3 = B_0 + B_1$

10

 

Question [2]: [25 marks]


a. Realize the following set of Boolean equations using ROM implementation:

$$x_0(a, b, c) = c$$

$$x_1(a, b, c) = b$$

$$x_2(a, b, c) = a$$

 Tabulate the truth table for the ROM, and then draw the circuit implementation of the ROM, and show the fuse mapping. **[15 marks]**




Truth Table
for the ROM

ROM Circuit Implementation



a. Realize the following function using three state buffers and any additional logic gates, and use A as a control signal: **[10 marks]**

$$F(A, B, C) = \overline{A}BC + A$$

 


Question [3]: [25 mark]

  - a. The JK-FF module given in figure (1) with a rising edge of the clock "clk", asynchronous active high "clear", and asynchronous active low "PreN". The output for JK-FF is Q. Figure (2) gives some forces for the inputs, Sketch the outputs Q. [15 marks]




- a. Explain how to convert a single J-K flip flop to T-flip flop. Show all of your steps. Draw the converted J-K flip flop with any additional gates. [10 marks]

Q	Q'	J	K	T
0	0	0	x	0
0	1	1	x	1
1	0	x	1	1
1	1	x	0	0

 


$$J = T$$

(3)

 

$$K = T$$

(3)

 


(4)

Question [4]: [25 mark]

Using falling-edge triggered D flip-flops, design a counter with the following repeated binary sequence: 0, 1, 2, 4, 6.

- Draw the logic diagram of the counter
- What will happen if the counter is started in state 011.

C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	-	-	-
1	0	0	1	1	0
1	0	1	-	-	-
1	1	0	0	0	0
1	1	1	-	-	-

 

C	B	A
00	0	1
01	0	X
11	X	X
10	1	0

C	B	A
00	0	1
01	1	X
11	X	X
10	0	0


C	B	A
00	1	0
01	0	X
11	X	X
10	0	0

$$D_C = C^+ = \bar{B}C + B\bar{C} = B \oplus C$$

$$D_B = B^+ = \bar{B}C + A$$

$$D_A = A^+ = \bar{A}\bar{B}\bar{C}$$

(a)

 

(b)

